

# Sequential Logic (con't)

## (Class 3.1 – 2/2/2021)

CSE 4357/CSE 5357 – Advanced Digital Logic Design  
Spring 2021

*Instructor – Bill Carroll, PhD, PE, Professor*



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Today's Topics

- Course calendar
- Counters
- Clock dividers
- Basic timers
- Registers
- Register files
- Assignment #2 posted – due 2/6/21, 11:59 PM



# Course Calendar

Week	Suggested Reading	Class date	Tuesday (1) Lecture Topics	Class date	Thursday (2) Lecture Topics	Assignment	Due Date (11:59 PM)
1	Ciletti, Chs 1, 2 and 4	1/19	Course overview. Programmable logic. Review of combinational logic and Verilog.	1/21	Review of combinational logic and Verilog (continued).	Check out DE1-SoC development kit.	1/22
2	Ciletti, Chs 3 and 5	1/26	Using Quartus Prime 18.1. High-speed adders.	1/28	Review of sequential logic and Verilog -- recognizers.	Assignment 1 -- Ripple-Carry Adder/Subtractor	1/30
3	Ciletti, Chs 3 and 5	2/2	Review of sequential logic and Verilog -- registers and counters.	2/4	Review of sequential logic and Verilog -- controllers. Logic hazards.	Assignment 2 -- Knight Rider.	2/6
4	Ciletti, Chs 4 and 6	2/9	Test benches.	2/11	ModelSim.	Assignment 3 -- Test Bench for RAddSub.	2/13
5	Ciletti, Chapter 8	2/16	FPGA organization and architecture.	2/18	Quartus Prime processes.	None	2/20
6		2/23	Examination 1 (SH 103)	2/25	Quartus Prime analysis tools.	Assignment 4 -- Two-function High-speed ALU.	2/27
7	Ciletti, Chapter 10	3/2	Basic multipliers.	3/4	High-speed multipliers.	TBA	
8	Ciletti, Chapter 10	3/9	High-speed multipliers (continued)	3/11	High-speed multipliers (continued)	TBA	
SB		3/16	Spring Break	3/18	Spring Break		
9	Lee, Chapter 8	3/23	Pipelined functional units.	3/25	Pipelined functional units (continued).	TBA	
10	Ciletti, Chapter 10	3/30	Dividers.	4/1	Dividers (continued).	TBA	
11	Ciletti, Chapter 11	4/6	Examination 2 (SEIR 194)	4/8	Post-synthesis design tasks.	TBA	
12	Ciletti, Chapter 11	4/13	Timing analysis.	4/15	Timing analysis (continued).	TBA	
13	Ciletti, Chapter 7	4/20	ALU design.	4/22	ALU design (continued).		
14		4/27	Project work	4/29	Project work		
15		5/4	Project work				



UNIVERSITY OF  
TEXAS  
ARLINGTON


DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# *Counters*



 
# Binary Counter

- Counters – sequential circuits that tally, or count, in a predetermined code sequence, the number of input pulses received, e.g., 3-bit binary counter.



# States =  $2^n$

 

UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Binary Counter Verilog Model

```
// Behavioral model of a three-bit binary counter
module binarycounter (COUNT, CLEAR, y);
input COUNT, CLEAR;
output reg [2:0] y;           // y is defined as a 3-bit output register
    always @ (posedge COUNT, negedge CLEAR)
        if (CLEAR) y <= 3'b0; // y is loaded with binary 000
        else
            begin
                if (y == 3'b111)
                    y <= 3'b0; // Once y = 111 it is cleared
                else
                    y <= y + 1'b1; // y is incremented
            end
    end
endmodule
```



# *n*-Bit Binary Counters

// n-bit binary counter



```
module NbitBinCount (COUNT,CLEAR,y);  
    parameter N=4;  
    input COUNT, CLEAR;  
    output reg [N-1:0] y;           // y is defined as a register  
    always @ (posedge COUNT, negedge CLEAR)  
        if (CLEAR==1'b0) y <= 0;   // y is loaded with all 0's  
        else  
            begin  
                if (y == 2**N-1'b1) y <= 0;   // Once y = 2**N-1 it is cleared  
                else y <= y + 1'b1;           // y is incremented  
            end  
endmodule
```



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Binary Up/Down Counter

  

UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING



# Binary Up/Down Counter

// Behavioral n-bit binary up/down counter. Positive-edge triggered. Active-low clear.

```
module BinaryUpDown (CLK, CLEAR, UP, COUNT);
```

```
    parameter N = 3'd3;
```

```
    input CLK, CLEAR, UP;
```

```
    output reg [N-1:0] COUNT;
```

```
    always @ (posedge CLK, negedge CLEAR)
```

```
        if (CLEAR==0) COUNT <= 0;
```

```
    else
```

```
        if (UP==0)
```

```
            COUNT <= COUNT + 1'b1;
```

```
        else
```

```
            COUNT <= COUNT - 1'b1;
```

```
endmodule
```

//COUNT is defined as an N-bit register

//trigger on clock or clear

//COUNT is loaded with binary all 0's

//count up or down?

//count up

//count down




UNIVERSITY OF  
TEXAS  
ARLINGTON


DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Divide-By Counters

Divide-by-10

 

Divide-by-6

 

# Divide-By-N Counter

// Divide by 10 counter

```
module divideX10 (CLK,CLEAR,OUT,COUNT);
```

```
    parameter N=4'd10;
```

```
    input CLK, CLEAR;
```

```
    output reg [3:0] COUNT;
```

// COUNT is defined as a 4-bit register

```
    output reg OUT;
```

```
    always @ (negedge CLK, negedge CLEAR)
```

```
        if (CLEAR==1'b0)    COUNT <= 4'b0;
```

// COUNT is loaded with all 0's

```
        else
```

```
        begin
```

```
            if (COUNT == N-2'd2) begin OUT <= 1'b1; COUNT <= N-1'd1; end // Once COUNT = N-2 OUT = 1
```

```
            else
```

```
            if (COUNT == N-1'd1) begin OUT <= 1'b0; COUNT <= 4'b0; end //Once COUNT = N-1 OUT=0
```


```
            else begin OUT <= 1'b0; COUNT <= COUNT + 1'b1; end // COUNT is incremented
```

```
        end
```


```
endmodule
```




# Divide-By- $N$ Counter, $N=10$

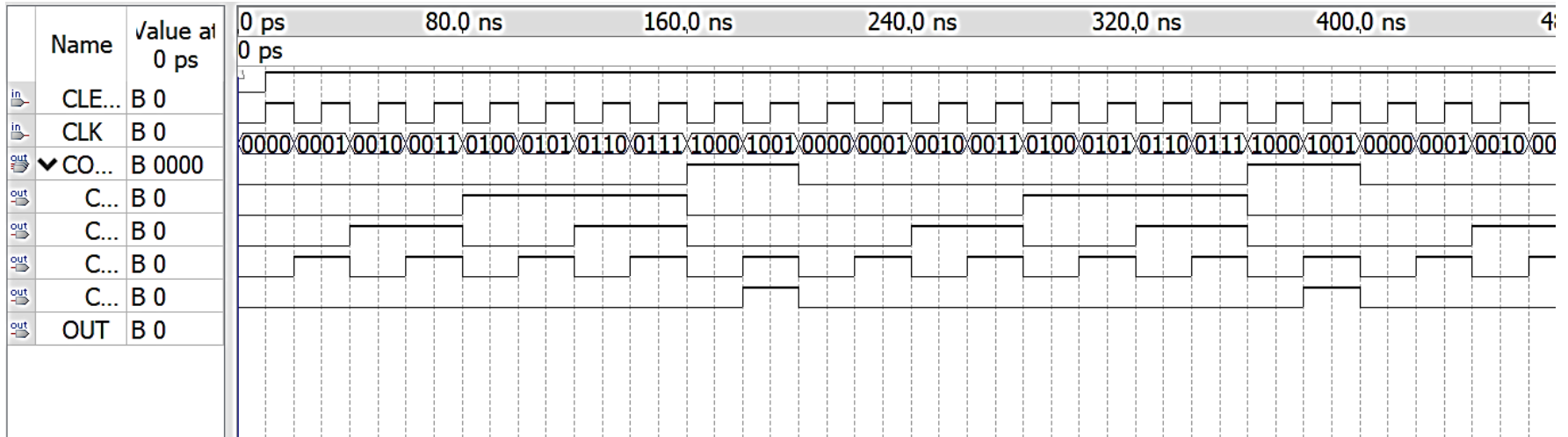


# 0 to 59 Second Timer

 



# Digital Timer Design

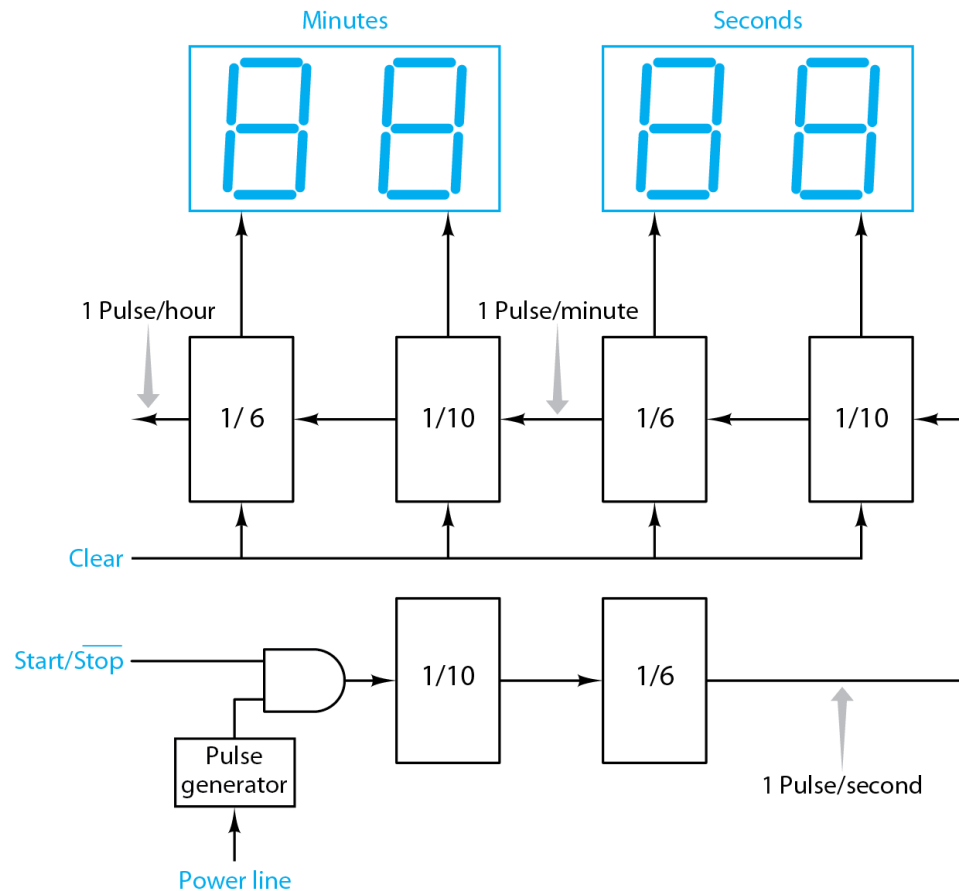

# Digital Timer Design (revisited)

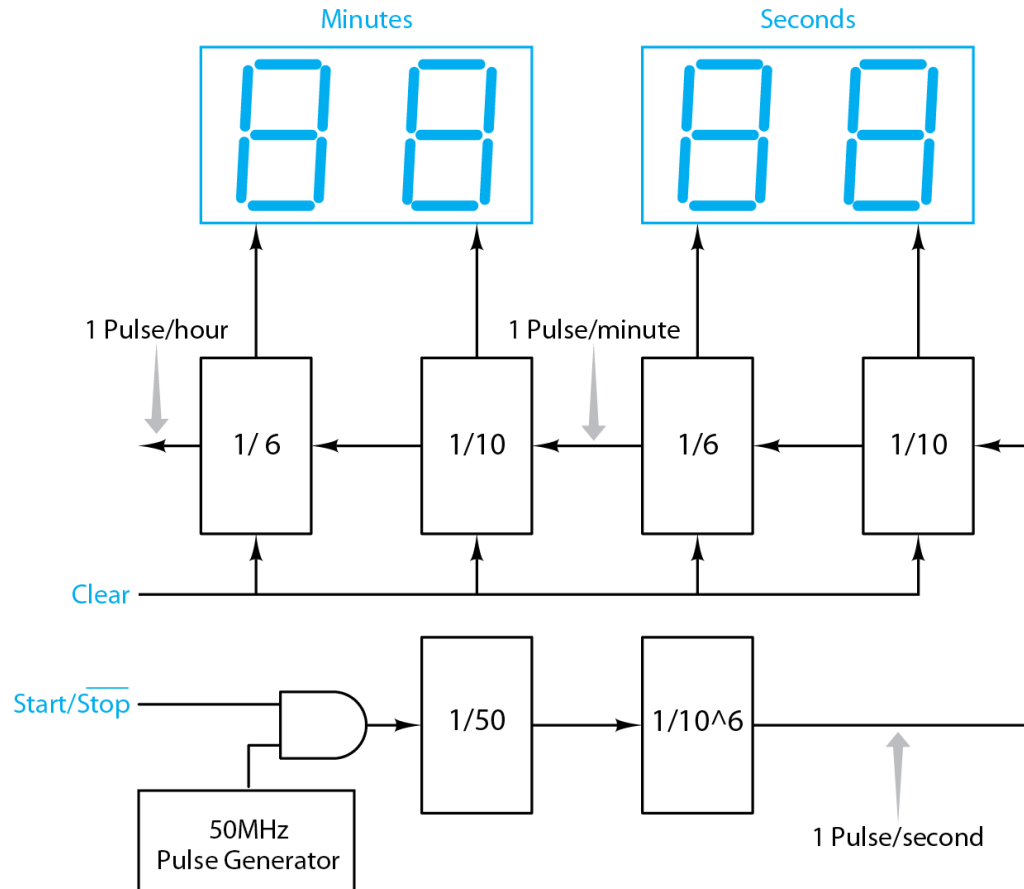

# Divide-by-50x10<sup>6</sup> Counter

  



# Frequency References

Power line – 60 Hz or 50 Hz

Crystal oscillators – various frequencies available

Phased-locked-loops – widely used (DE1-SoC has six)

CLOCK\_50 – PIN\_AF14

CLOCK2\_50 – PIN\_AA16

CLOCK3\_50 – PIN\_Y26

CLOCK4\_50 – PIN\_K14

All 50-MHz



# Divide-By-Six Counter

// Divide by Six counter

```
module divideX6 (CLK,CLEAR,OUT,COUNT);
```

```
    parameter N=3'd6;
```

```
    input CLK, CLEAR;
```

```
    output reg [2:0] COUNT;
```

// COUNT is defined as a 3-bit register

```
    output reg OUT;
```

```
    always @ (negedge CLK, negedge CLEAR)
```

```
        if (CLEAR==1'b0)    COUNT <= 3'b0;
```

// COUNT is loaded with all 0's

```
        else
```

```
        begin
```

```
            if (COUNT == N-2'd2) begin OUT <= 1'b1; COUNT <= N-1'd1; end // Once COUNT = N-2 OUT = 1
```

```
            else
```

```
                if (COUNT == N-1'd1) begin OUT <= 1'b0; COUNT <= 3'b0; end //Once COUNT = N-1 OUT=0
```

```
                else begin OUT <= 1'b0; COUNT <= COUNT + 1'b1; end // COUNT is incremented
```

```
        end
```

```
endmodule
```



# Divide-By-10 Counter

// Divide by 10 counter

```
module divideX10 (CLK,CLEAR,OUT,COUNT);
```

```
    parameter N=4'd10;
```

```
    input CLK, CLEAR;
```

```
    output reg [3:0] COUNT;
```

// COUNT is defined as a 4-bit register

```
    output reg OUT;
```

```
    always @ (negedge CLK, negedge CLEAR)
```

```
        if (CLEAR==1'b0)    COUNT <= 4'b0;
```

// COUNT is loaded with all 0's

```
        else
```

```
        begin
```

```
            if (COUNT == N-2'd2) begin OUT <= 1'b1; COUNT <= N-1'd1; end // Once COUNT = N-2 OUT = 1
```

```
            else
```

```
            if (COUNT == N-1'd1) begin OUT <= 1'b0; COUNT <= 4'b0; end //Once COUNT = N-1 OUT=0
```

```
            else begin OUT <= 1'b0; COUNT <= COUNT + 1'b1; end // COUNT is incremented
```

```
        end
```

```
endmodule
```



# Divide-By-Five Counter

// Divide by Five counter

```
module divideX5 (CLK,CLEAR,OUT,COUNT);
```

```
    parameter N=3'd5;
```

```
    input CLK, CLEAR;
```

```
    output reg [2:0] COUNT;
```

// COUNT is defined as a 3-bit register

```
    output reg OUT;
```

```
    always @ (negedge CLK, negedge CLEAR)
```

```
        if (CLEAR==1'b0)    COUNT <= 3'b0;
```

// COUNT is loaded with all 0's

```
        else
```

```
        begin
```

```
            if (COUNT == N-2'd2) begin OUT <= 1'b1; COUNT <= N-1'd1; end // Once COUNT = N-2 OUT = 1
```

```
            else
```

```
                if (COUNT == N-1'd1) begin OUT <= 1'b0; COUNT <= 3'b0; end //Once COUNT = N-1 OUT=0
```

```
                else begin OUT <= 1'b0; COUNT <= COUNT + 1'b1; end // COUNT is incremented
```

```
        end
```

```
endmodule
```



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Divide-By-1000 Counter

// Divide by 1000 counter

```
module divideX1000 (CLK,CLEAR,OUT,COUNT);
```

```
    parameter N=10'd1000;
```

```
    input CLK, CLEAR;
```

```
    output reg [9:0] COUNT;
```

// COUNT is defined as a 10-bit register

```
    output reg OUT;
```

```
    always @ (negedge CLK, negedge CLEAR)
```

```
        if (CLEAR==1'b0)    COUNT <= 10'b0;
```

// COUNT is loaded with all 0's

```
        else
```

```
        begin
```

```
            if (COUNT == N-2'd2) begin OUT <= 1'b1; COUNT <= N-1'd1; end // Once COUNT = N-2 OUT = 1
```

```
            else
```

```
                if (COUNT == N-1'd1) begin OUT <= 1'b0; COUNT <= 10'b0; end //Once COUNT = N-1 OUT=0
```

```
                else begin OUT <= 1'b0; COUNT <= COUNT + 1'b1; end // COUNT is incremented
```

```
        end
```

```
endmodule
```



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Digital Timer Verilog Code

```
//Zero to 59 second timer
module timerdemo
(
    input clock, reset,
    output [0:6] Aout, Bout
);
    wire [3:0] A, B;
    wire five, ten, k1, k0, sec0, sec1;
    wire [3:0] count5, count10;
    wire [9:0] count1000L, count1000M;
//instantiations
divideX5 div5
(
    .CLK(clock) ,           // input  50MHz clock
    .CLEAR(reset) ,         // input  reset
    .OUT(five) ,            // output  every 5 input pulses
    .COUNT(count5)        // output [3:0] count bits
);
divideX10 div10
(
    .CLK(five) ,           // input  10MHz clock
    .CLEAR(reset) ,         // input  reset
    .OUT(ten) ,            // output  every 10 input pulses
    .COUNT(count10)       // output [3:0] count bits
);
divideX1000 div1000M
(
    .CLK(ten) , // input  1MHz clock
    .CLEAR(reset) , // input  reset
    .OUT(k1) , // output  every 1000 input pulses
    .COUNT(count1000M) // output [9:0] count bits
);
```



# Digital Timer Verilog Code


```
divideX1000 div1000L
(
    .CLK(k1), // input 1KHz clock
    .CLEAR(reset), // input reset
    .OUT(k0), // output 1000 input pulses
    .COUNT(count1000L) // output [9:0] count bits
);
divideX10 seconds_low
(
    .CLK(k0), // input 1Hz clock
    .CLEAR(reset), // input reset
    .OUT(sec0), // output every 10 input pulses
    .COUNT(B) // output [3:0] seconds low count
);
binary2seven seconds_low_display
(
    .BIN(B), // input [3:0] seconds low count
    .SEV(Bout) // output [0:6] low seconds display
);
divideX6 seconds_high
(
    .CLK(sec0), // input from low seconds
    .CLEAR(reset), // input CLEAR_sig
    .OUT(sec1), // output to low minutes
    .COUNT(A) // output [3:0] high seconds count
);
binary2seven seconds_high_display
(
    .BIN(A), // input [3:0] high seconds count
    .SEV(Aout) // output [0:6] high seconds display
);
endmodule
```


 
# OnOff-Toggle Latch



If  $\text{CLR} = 0$ ,  $\text{OUT} = 0$ . Otherwise,  $\text{OUT} = \text{IN}$  when toggled *On* and  $\text{OUT} = 0$  when toggled *Off*.





# Verilog OnOff-Toggle Latch

*//OnOff Toggle Latch. Assumes an normally-on push button switch for OnOff.*



```
module ToggleLatch (OnOff, CLR, IN, OUT);  
input OnOff, IN, CLR;  
output OUT;  
reg state, nextstate;  
parameter ON=1'b1, OFF=1'b0;  
    always @ (negedge OnOff, negedge CLR) //Active-low CLR.  
        if (CLR==1'b0) state <= OFF;           //CLR turns the switch off.  
        else state <= nextstate;  
    always @ (state)  
        case(state)  
            OFF: nextstate = ON;           //Pushing OnOff turns the switch on.  
            ON: nextstate = OFF;          //Pushing OnOff turns the switch off.  
        endcase  
    assign OUT = state*IN; //Out = In when switch in on. Otherwise, Out = 0.  
endmodule
```



# *Registers*



# Basic Register

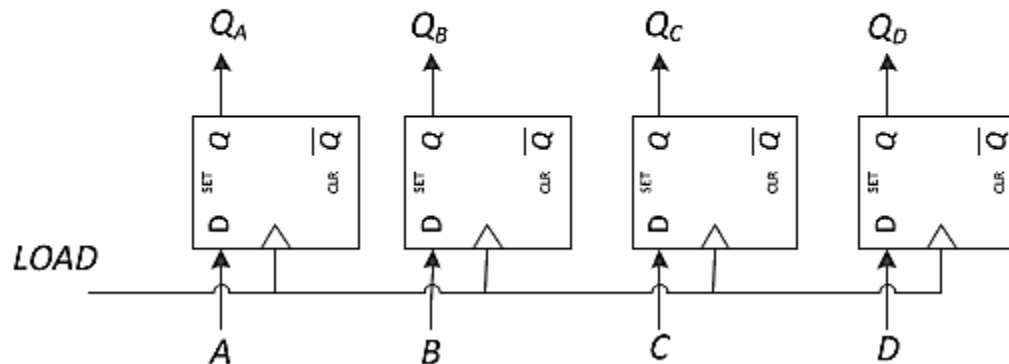
 


# Basic Register – Verilog Model

```
//Verilog Model of an N-bit register with active-low asynchronous clear
module NbitRegister (D,Q,CLK,CLR);
    parameter N = 4;           //declare default value for N
    input [N-1:0] D;           //declare N-bit data input
    input CLK, CLR;            //declare clock and clear inputs
    output reg [N-1:0] Q;       //declare N-bit data output
    always @ (posedge CLK, negedge CLR) //detect change of clock or clear
        begin
            if (CLR==1'b0) Q <= 0;           //register loaded with all 0's
            else if (CLK==1'b1) Q <= D;       //data input values loaded in register
        end
endmodule
```



# Serial-In/Serial-Out Register

 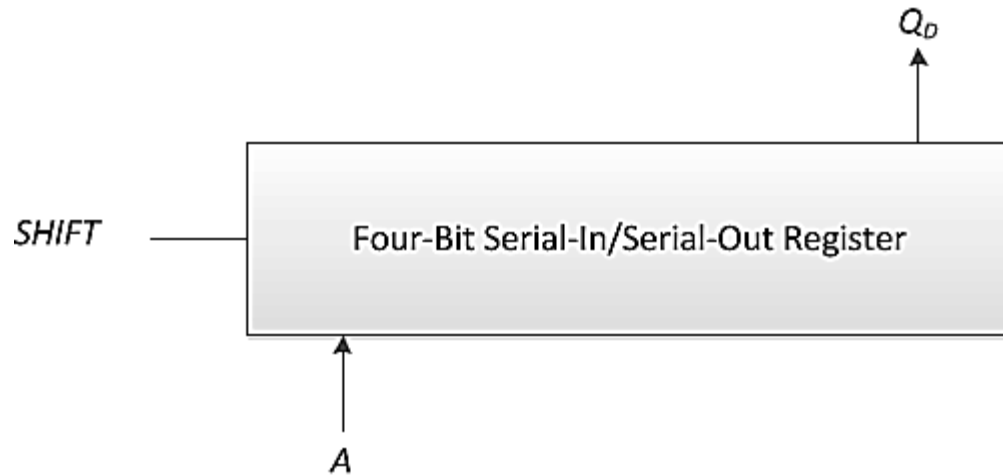


# Serial-In/Serial-Out Register – Verilog

```
//Verilog Model of an N-bit Serial-In Serial-Out Shift Register with active-low clear
module NbitSerialInSerialOut (A,Q,SHIFT,CLR);
    parameter N = 4;           //declare default value for N
    input A;                   //declare data input
    input SHIFT, CLR;          //declare shift and clear inputs
    output reg [N-1:0] Q;       //declare N-bit data output
    integer i;                 //declare index variable
    always @ (posedge SHIFT, negedge CLR) //detect change of clock or clear
    begin
        if (CLR==1'b0) Q <= 0; //register loaded with all 0's
        else if (SHIFT==1'b1)
        begin //shift and load input A
            for (i = 1; i <= N-1; i = i + 1)
                begin Q[i] <= Q[i-1]; Q[0] <= A; end
            end
        end
    end
endmodule
```



# Multifunction Registers

*N-Bit Register/Counter*

 

(a)

<i>RST</i>	<i>CE</i>	<i>M1</i>	<i>M0</i>	<i>Q+</i>	<i>Function</i>
1	x	x	x	$Q_i^+ \leq 0$	<i>Reset</i>
0	0	x	x	$Q_i^+ \leq Q$	<i>Hold</i>
0	1	0	0	$Q_i^+ \leq Q$	<i>Hold</i>
0	1	0	1	$Q_i^+ \leq Q_{i+1}$	<i>Shift</i>
0	1	1	0	$Q^+ \leq Q+1$	<i>Count</i>
0	1	1	1	$Q^+ \leq Din$	<i>Load</i>

(b)

## *Input/Output Signals*

*Din* – *N*-bit data input.

*Q* – *N*-bit data output.

*CE* – Active-high clock enable.

*M* – 2-bit function code (*M1*, *M0*).

*RST* – Active-high asynchronous reset.

*CLK* – Active-high clock. Triggers operations on the rising edge.

## *Function Table*



# Multifunction Registers

//Verilog model of an N-bit multifunction register

```
module register #(parameter N = 4)
(
  input CLK, RST, CE,           //declare clock, reset, and clock enable inputs
  input [1:0] M,                //declare function inputs
  input [N-1:0] Din,           //declare data inputs
  output reg [N-1:0] Q          //declare data outputs
);
  always @ (posedge CLK or posedge RST) begin
    if (RST) Q <= 0;            //reset detected
    else if (CE) begin          //check for clock enable
      if (M == 2'b01) Q <= Q >> 1'b1; //right shift
      else if (M == 2'b10) Q <= Q + 1'b1; //increment
      else if (M == 2'b11) Q <= Din; //load
    end
  end
endmodule
```




UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING




# Multifunction Register Simulation

 


UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Register File

 

$n$ -bit x  $N$  Register File

 

Input/Output Diagram ( $N = 4$ )

$DIN$  – data input ( $n$ -bits)

$DOUT$  – data output ( $n$ -bits)

$WA$  – write address (2-bits)

$RA$  – read address (2-bits)


$WrEn$  – write enable (1-bit)



# Register File Organization

Register with Clock Enable

Two-to-four decoder  
with Enable

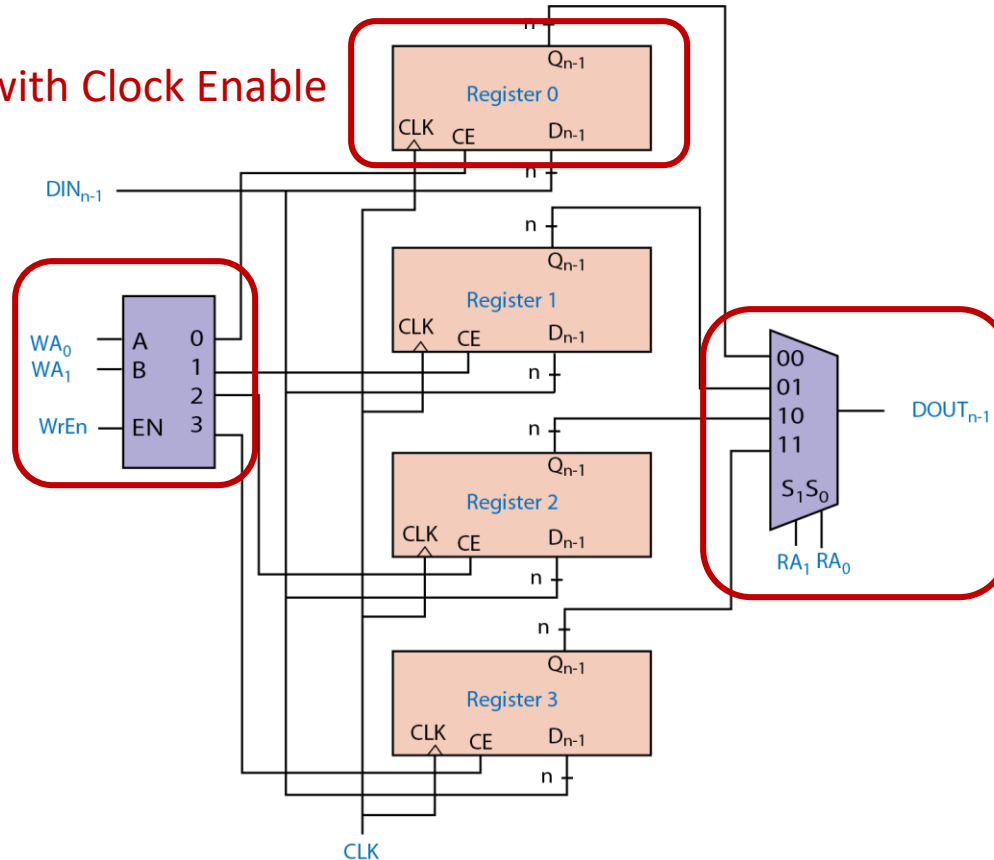

Four-to-one  
 $n$ -bit multiplexer



UNIVERSITY OF  
TEXAS  
ARLINGTON


DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Two-to-Four Decoder with Enable

```
//Two to Four Active High Decoder with Enable
module Two2FourActiveHigh (
    input A,B,E,
    output reg [3:0] y);
    always @ (A, B, E)
        if (~E) y = 4'b0; //output all 0's if not enabled
        else
            case ({B,A}) //decode input if enabled
                2'b00: y = 4'b0001;
                2'b01: y = 4'b0010;
                2'b10: y = 4'b0100;
                2'b11: y = 4'b1000;
            endcase
    endmodule
```



# Two-to-Four Decoder Simulation

 

# $n$ -bit Register with Clock Enable

Recall

```
//Verilog Model of an N-bit register with active-low asynchronous clear
module NbitRegister (D,Q,CLK,CLR);
    parameter N = 4;           //declare default value for N
    input [N-1:0] D;           //declare N-bit data input
    input CLK, CLR;            //declare clock and clear inputs
    output reg [N-1:0] Q;       //declare N-bit data output
    always @ (posedge CLK, negedge CLR) //detect change of clock or clear
    begin
        if (CLR==1'b0) Q <= 0; //register loaded with all 0's
        else if (CLK==1'b1) Q <= D; //data input values loaded in register
    end
endmodule
```



# *n*-bit Register with Clock Enable

//Verilog Model of an N-bit register with active-low clear and clock enable

```
module NbitRegister (  
    input [N-1:0] D;           //declare N-bit data input  
    input CLK, CLR, CE,       //declare clock, clear, and clock enable inputs  
    output reg [N-1:0] Q;      //declare N-bit data output  
    parameter N = 4;          //declare default value for N  
    always @ (posedge CLK, negedge CLR) //detect change of clock or clear  
    begin  
        if (CLR==1'b0) Q <= 0; //register loaded with all 0's  
        else if (CLK&CE==1'b1) Q <= D; //data input values loaded in register  
        else Q <= Q; // hold current values if not enabled  
    end  
endmodule
```




# Four-bit Register Simulation

Simulation Waveform Editor - C:/Users/Bill/Dropbox/NbitRegisterWEnable/NbitRegisterWEnable - NbitRegisterWEnable - [NbitRegisterWEnable\_20200909200730.sim.vwf (Read-Only)]

File Edit View Simulation Help

Search altera.c

 

UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING



# Four-to-One $n$ -Bit Multiplexer

```
//Four-to-one, N-bit multiplexer
module four2one #(parameter N = 4)
(
    input A,B,                //declare select inputs
    input [N-1:0] D0,D1,D2,D3, //declare data inputs
    output reg [N-1:0] Y       //declare data outputs
);
    always @ (A,B,D0,D1,D2,D3) //detect input change
        case ({B,A})           //derive the output
            2'b00: Y = D0;
            2'b01: Y = D1;
            2'b10: Y = D2;
            2'b11: Y = D3;
        endcase
endmodule
```




# Four-to-One Multiplexer Simulation

Simulation Waveform Editor - C:/Users/Bill/Dropbox/four2one/four2one - four2one - [four2one\_20200909200026.sim.vwf (Read-Only)]

File Edit View Simulation Help

Search alt

 

UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Instantiation Revisited

```
//Use of instances of binary2seven decoder module
module instances
(
    input [3:0] A, B,           //A:SW7,SW6,SW5,SW4; B:SW3,SW2,SW1,SW0
    output [0:6] outA, outB     //outA:HEX1; outB:HEX0
);
    binary2seven hex0 //By position
    (
        B,               // input [3:0] B
        outB              // output [0:6] outB
    );
    binary2seven hex1 //By name
    (
        .BIN(A) ,         // input [3:0] A
        .SEV(outA)        // output [0:6] outA
    );
endmodule
```



# Instantiation Revisited

//Register 0

NbitRegisterWEnable R0                      //By position

```
(  
    .D(Din) ,        // input [3:0] Din  
    .CLK(CLK) ,     // input CLK  
    .CLR(RST) ,     // input RST  
    .CE(y[0]) ,     // input y[0]  
    .Q(Q0)          // output [3:0] Q0  
);
```


//Register 1

NbitRegisterWEnable R1                      //By name

```
(  
    .D(Din) ,        // input [3:0] Din  
    .CLK(CLK) ,     // input CLK  
    .CLR(RST) ,     // input RST  
    .CE(y[1]) ,     // input y[1]  
    .Q(Q1)          // output [3:0] Q1  
);
```



# Register File Organization

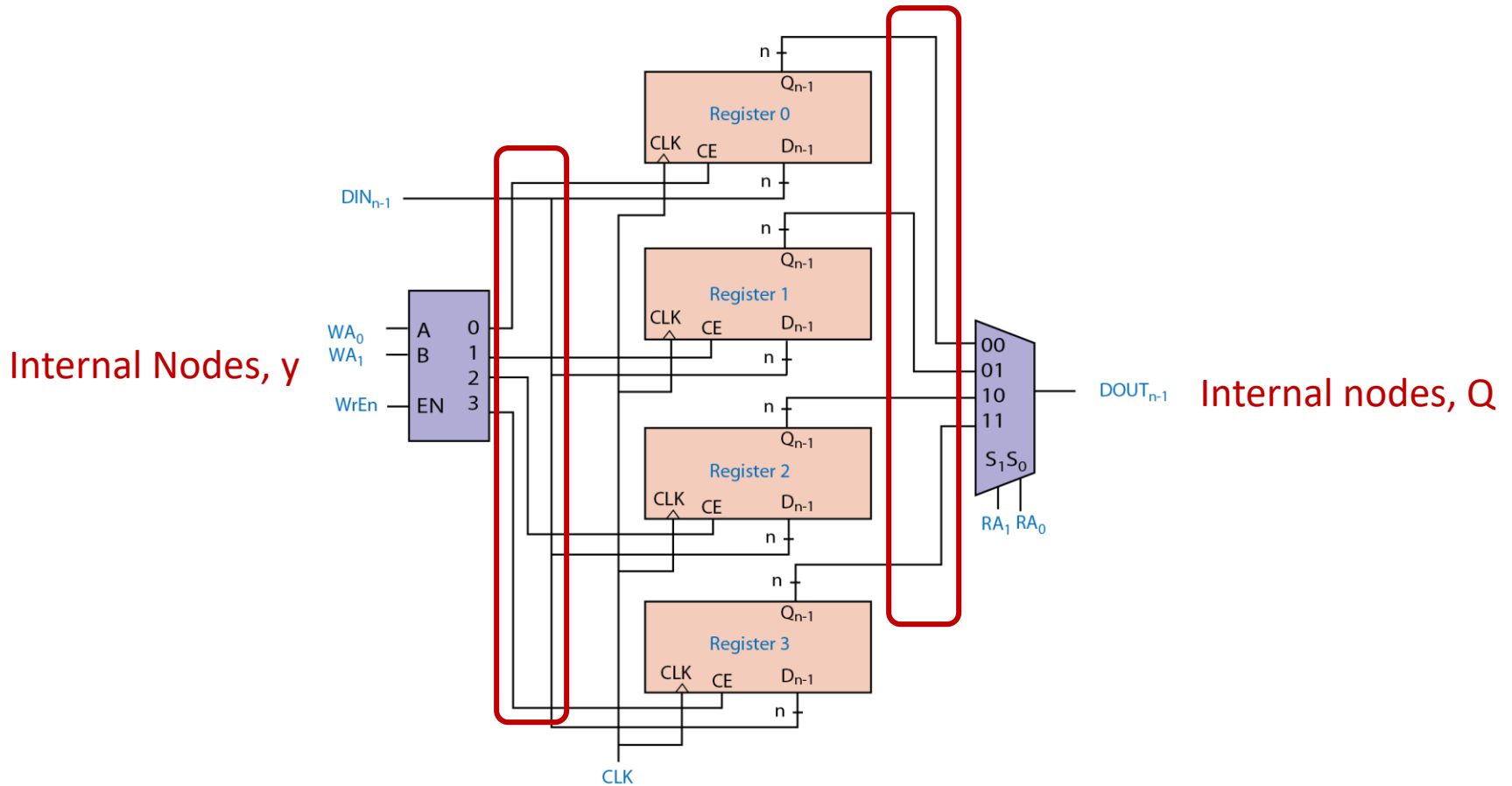

# Interconnecting Modules

Define internal nodes

```
wire [3:0] Q3, Q2, Q1, Q0, y;
```



# Four-to-One $n$ -Bit Multiplexer

```
//Four-to-one, N-bit multiplexer
module four2one #(parameter N = 4)
(
    input A,B,                //declare select inputs
    input [N-1:0] D0,D1,D2,D3, //declare data inputs
    output reg [N-1:0] Y       //declare data outputs
);
    always @ (A,B,D0,D1,D2,D3) //detect input change
        case ({B,A})           //derive the output
            2'b00: Y = D0;
            2'b01: Y = D1;
            2'b10: Y = D2;
            2'b11: Y = D3;
        endcase
endmodule
```



# *Pin Assignments Revisited*





# Pin Assignments Revisited

- Assignments Editor – manual
- Pin Planner
- TCL (Tool Command Language) console
- Import .QSF (Quartus Settings File) files



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Pin Assignments Revisited

//Slide switches to LEDs

```
module switch2led
(
    input [9:0] SW,
    output [9:0] LEDR
);
    assign LEDR = SW;
endmodule
```

SW0 – PIN_AB12	LEDR0 – PIN_V16
SW1 – PIN_AC12	LEDR1 – PIN_W16
SW2 – PIN_AF9	LEDR2 – PIN_V17
SW3 – PIN_AF10	LEDR3 – PIN_V18
SW4 – PIN_AD11	LEDR4 – PIN_W17
SW5 – PIN_AD12	LEDR5 – PIN_W19
SW6 – PIN_AE11	LEDR6 – PIN_Y19
SW7 – PIN_AC9	LEDR7 – PIN_W20
SW8 – PIN_AD10	LEDR8 – PIN_W21
SW9 – PIN_AE12	LEDR9 – PIN_Y21

set\_location\_assignment <pin#> -to <name>



# Pin Assignments Revisited

//Behavioral Verilog model of a digital lock. Code 110010.

module toplock (

input [9:0] SW, //Declare slide switch inputs  
input [3:0] KEY, //Declare pushbutton inputs  
output [9:0] LEDR, //Declare LED outputs  
output [0:6] HEX0; //Declare HEX0 output

reg Open; //Declare lock Open output  
reg [2:0] state, nextstate; //Declare lock state variables  
wire [0:6] stateout; //Declare lock state output  
wire x, Enter, ResetLock; //Declare lock inputs

parameter A=3'b000,B=3'b001,C=3'b010,D=3'b011,E=3'b100,F=3'b101,G=3'b110,H=3'b111;

assign ResetLock = KEY[0]; //Map lock inputs & outputs to switches and LEDs  
assign Enter = KEY[1];  
assign x = SW[1];  
assign LEDR[0] = Open;  
assign LEDR[1] = SW[1];  
assign HEX0 = stateout;

always @ (negedge Enter, negedge ResetLock) //Begin lock behavioral model  
if (ResetLock == 1'b0) state <= A;  
else state <= nextstate;



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# Pin Assignments Revisited

```
always @ (state, x)
    case (state)
        A: if (~x) nextstate = H; else nextstate = B;
        B: if (~x) nextstate = H; else nextstate = C;
        C: if (~x) nextstate = D; else nextstate = H;
        D: if (~x) nextstate = E; else nextstate = H;
        E: if (~x) nextstate = H; else nextstate = F;
        F: if (~x) nextstate = G; else nextstate = H;
        G: nextstate = G;
        H: nextstate = H;
    endcase
always @ (state, x)
    case (state)
        A,B,C,D,E,F,H: Open = 1'b0;
        G: Open = 1'b1;
    endcase
//
binary2seven binary2seven_inst
(
    .BIN(state), // input [3:0] state
    .SEV(stateout) // output [0:6] stateout
);
endmodule
```



# Assignment #2 Preview

Design, implement, and demonstrate a Knight Rider Flasher.



- ✓ Clock\_50 50-MHz clock
- ✓ On/Off toggle
- ✓ Clock divider
- ✓ Up/Down counter
- ✓ Module instantiation
- ✓ Pin assignment

Due – February 6, 2021, 11:59 PM



UNIVERSITY OF  
TEXAS  
ARLINGTON

DEPARTMENT OF  
COMPUTER SCIENCE  
AND ENGINEERING

# *Q & A*

