

Jorge Avila

Dr. Bill Carroll

Advanced Digital Logic

06 February 2021

Knight Rider Flash Report

Jorge Avila
James

Top Module:

```

module KnightRiderFlasher(

    // I will need CLOCK_50 -> PIN_AF14
    // On/Off Toggle Module
    // Clock Divider
    // Up/Down Counter
    // Module Instantiation
    // Pin Assignment -> The 0:9 LEDR on the DE1-Soc board

    input OnOff, //key1
    input Clock50, //clock_50
    output [9:0] LEDRArray); //the 10 LEDR on the board

    wire clock_toggle;
    wire clock_final;
    reg direction = 0; //direction where it will start
    wire [3:0] ledNumber;

    ToggleLatch toggy (OnOff,Clock50,clock_toggle);

    divideX d(clock_toggle,clock_final);

    UpDownCounter udc(clock_final,direction,OnOff,ledNumber);

    always @ (ledNumber)
        begin
            if(ledNumber == 15)
                direction = 0;
            if(ledNumber == 10)
                direction = 1;
        end

    decoder2N d2n(ledNumber,clock_toggle,LEDRArray);

endmodule

```

On-Off Toggle Module:

```
//OnOff Toggle Latch. Assumes an normally-on push button switch for
OnOff.
module ToggleLatch (
    input OnOff, IN,
    output OUT);

    reg state, nextstate;
    parameter ON= 1, OFF= 0;

    always @ (negedge OnOff)
        state <= nextstate;
    always @ (state)
        case(state)
            OFF: nextstate = ON;
            ON: nextstate = OFF;
            //CLR turns the switch off.
            //Pushing OnOff turns the switch on.
            //Pushing OnOff turns the switch off.
        endcase
    assign OUT = state&IN; //Out = In when switch in on. Otherwise,
    Out = 0.

endmodule
```

Clock-Divider Module:

```
module divideX (
    input CLK,
    output reg OUT);

    //parameter N = 5000000;
```

```

//parameter N = 2500000;
parameter N = 10000000;
reg [31:0] count;

always @ (negedge CLK)
begin
    count = count + 1;
    if(count >= (N-1))
        count = 0;
    if(count < (N/2))
        OUT = 1;
    else
        OUT=0;
end
endmodule

```

In this piece of code I just uncommented and re commented the different rates I wanted the LEDR to light up.

Demonstration:

The demonstration is this [LINK](#) here. It shows the different rates that were required in the lab report.

Pin Assignments:

<<new>>

☒
Filter on node names:

Category: All

	tatu	From	To	Assignment Name	Value	Enabled	Entity	Comment	Tag
1	✓		out LEDRArray[9]	Location	PIN_Y21	Yes			
2	✓		in OnOff	Location	PIN_AA15	Yes			
3	✓		out LEDRArray[1]	Location	PIN_W16	Yes			
4	✓		out LEDRArray[2]	Location	PIN_V17	Yes			
5	✓		out LEDRArray[3]	Location	PIN_V18	Yes			
6	✓		out LEDRArray[4]	Location	PIN_W17	Yes			
7	✓		out LEDRArray[5]	Location	PIN_W19	Yes			
8	✓		out LEDRArray[6]	LEDArray[5]	PIN_Y19	Yes			
9	✓		out LEDRArray[7]	Status: Ok	PIN_W20	Yes			
10	✓		out LEDRArray[8]	Location	PIN_W21	Yes			
11	✓		out LEDRArray[0]	Location	PIN_V16	Yes			
12	✓		in Clock50	Location	PIN_AF14	Yes			
13		<<new>>	<<new>>	<<new>>					

Full Code Below:

```
//Jorge Avila
//mavID: 1001543128
//Assignment #2

//This acts as the main code where everything will be called
module KnightRiderFlasher(

    // I will need CLOCK_50 -> PIN_AF14
    // On/Off Toggle Module
    // Clock Divider
    // Up/Down Counter
    // Module Instantiation
    // Pin Assignment -> The 0:9 LEDR on the DE1-Soc board

    input OnOff, //key1
    input Clock50, //clock_50
    output [9:0] LEDRArray); //the 10 LEDR

    wire clock_toggle;
    wire clock_final;
    reg direction = 0; //direction where it will start
```

```

    wire [3:0] ledNumber;

    ToggleLatch toggy (OnOff,Clock50,clock_toggle);

    divideX d(clock_toggle,clock_final);

    UpDownCounter udc(clock_final,direction,OnOff,ledNumber);

    decoder2N d2n(ledNumber,clock_toggle,LEDArray);

endmodule

//OnOff Toggle Latch. Assumes an normally-on push button switch for
OnOff.
module ToggleLatch (
    input OnOff, IN,
    output OUT);

    reg state, nextstate;
    parameter ON= 1, OFF= 0;

    always @ (negedge OnOff)
        state <= nextstate;
    always @ (state)
        case(state)
            OFF: nextstate = ON;
            ON: nextstate = OFF;
            //CLR turns the switch off.
            //Pushing OnOff turns the switch on.
//Pushing OnOff turns the switch off.
        endcase
    assign OUT = state&IN; //Out = In when switch in on. Otherwise,
    Out = 0.

endmodule

module divideX (

```

```

    input CLK,
    output reg OUT);

    //parameter N = 5000000;
    //parameter N = 2500000;
    parameter N = 10000000;
    reg [31:0] count;

    always @ (negedge CLK)
    begin
        count = count + 1;
        if(count >= (N-1))
            count = 0;
        if(count < (N/2))
            OUT = 1;
        else
            OUT=0;
    end
endmodule

module UpDownCounter(

    input CLK, UP, clr,
    output reg [N-1:0] COUNT);
    parameter N = 4;
    always @ (posedge CLK, negedge clr)
        if(clr == 0)
            COUNT <= 0; //clear this b
        else
            if (UP == 0)
                COUNT <= COUNT + 1;
            else
                COUNT <= COUNT - 1;

endmodule

//N to 2*N decoder - Bill Carroll's
module decoder2N #(parameter N = 4)

```

```
(input[N-1:0] in,  
input enable,output[2**N-1:0] out);  
assign out = (enable) ? (1 << in) : 0;  
endmodule
```